

Microarchitecture

(Single Cycle Processor)

Acknowledgment: Slides are adapted from Harris and Harris
textbook instructor's material

Introduction

- **Microarchitecture:** how to implement an architecture in hardware
- Processor:
 - **Datapath:** functional blocks
 - **Control:** control signals

Application Software	programs
Operating Systems	device drivers
Architecture	instructions registers
Micro-architecture	datapaths controllers
Logic	adders memories
Digital Circuits	AND gates NOT gates
Analog Circuits	amplifiers filters
Devices	transistors diodes
Physics	electrons

Microarchitecture

- Multiple implementations for the same architecture:
 - **Single-cycle:** Each instruction executes in a single cycle
 - **Multicycle:** Each instruction is broken into series of shorter steps
 - **Pipelined:** Each instruction broken up into series of steps & multiple instructions execute at once


RISC-V Processor

- Consider **subset** of RISC-V instructions:
 - R-type ALU instructions:
 - **add, sub, and, or, slt**
 - Memory instructions:
 - **lw, sw**
 - Branch instructions:
 - **beq**

Architectural State

- Defines the state of the program during execution
- Determines everything about a processor
- RISC-V elements include
 - PC
 - 32 registers
 - Memory
 - + specific control registers / flags
- Core dump file records architectural state at certain point in time

RISC-V Architectural State Elements

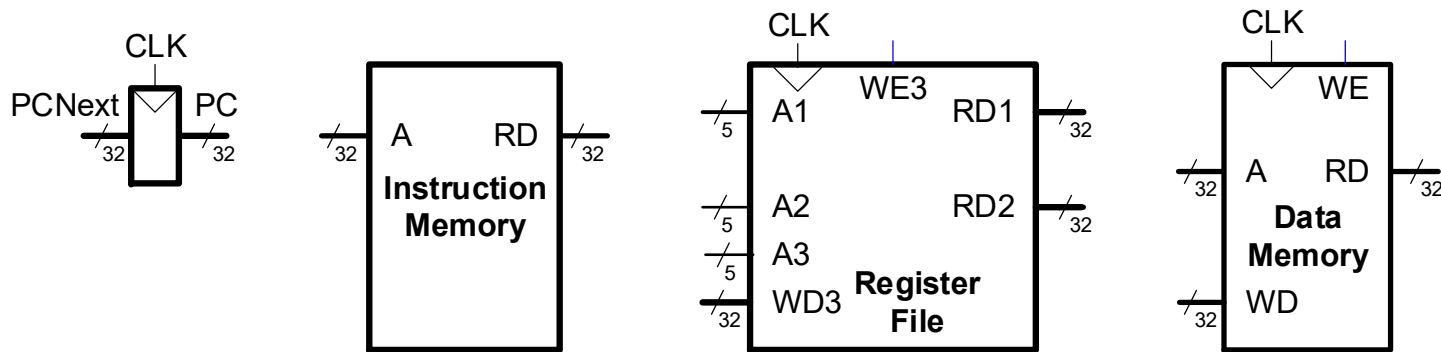

- Asynchronous read / synchronous write for memories
- Multi-ported register file
- Separate memory for instructions and data for now (will discuss how it fits store-program concept later)

Single-Cycle RISC-V Processor

- Datapath: Functional units where data are stored and processed
- Control: What generates control inputs to functional units

Example Program


- Design datapath
- View example program executing

Example Program:

Address	Instruction	Type	Fields					Machine Language	
0x1000	L7: lw x6, -4(x9)	I	imm _{11:0}	rs1	f3	rd	op	0000011	FFC4A303
0x1004	sw x6, 8(x9)	S	imm _{11:5}	rs2	rs1	f3	imm _{4:0}	op	0100011 0064A423
0x1008	or x4, x5, x6	R	funct7	rs2	rs1	f3	rd	op	0110011 0062E233
0x100C	beq x4, x4, L7	B	imm _{12,10:5}	rs2	rs1	f3	imm _{4:1,11}	op	1100011 FE420AE3


Single-Cycle Datapath: lw fetch

STEP 1: Fetch instruction

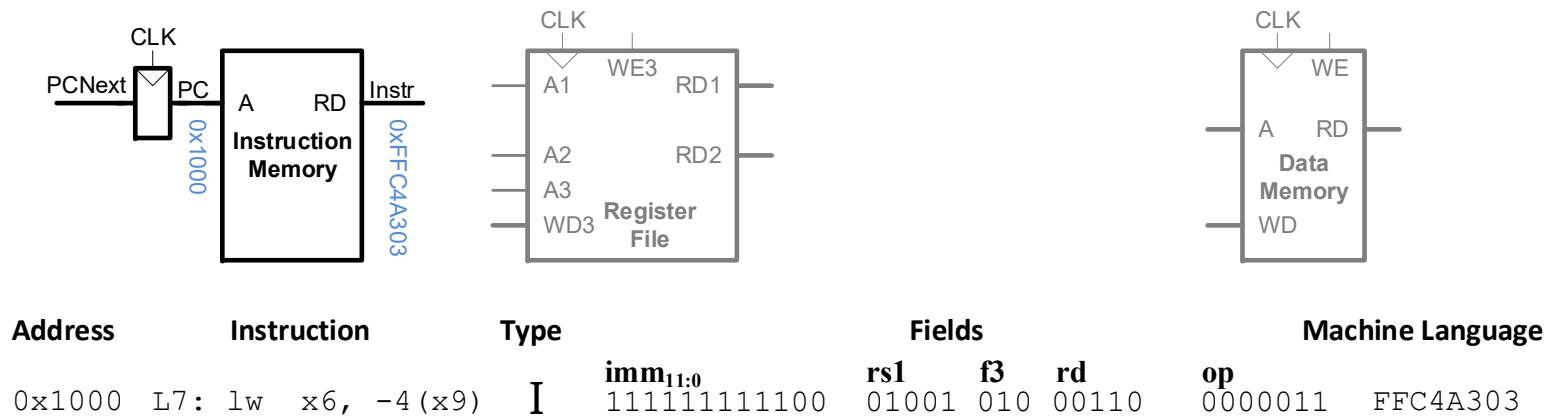

Single-Cycle Datapath: lw Reg Read

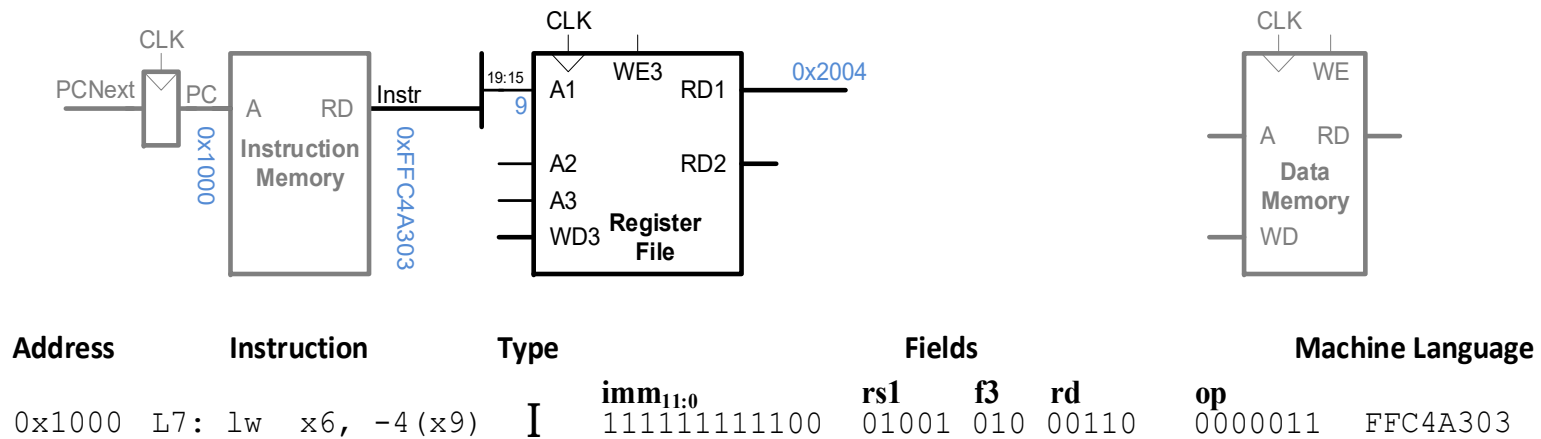
STEP 2: Read source operand (**rs1**) from RF



Single-Cycle Datapath: lw immediate

STEP 3: Extend the immediate

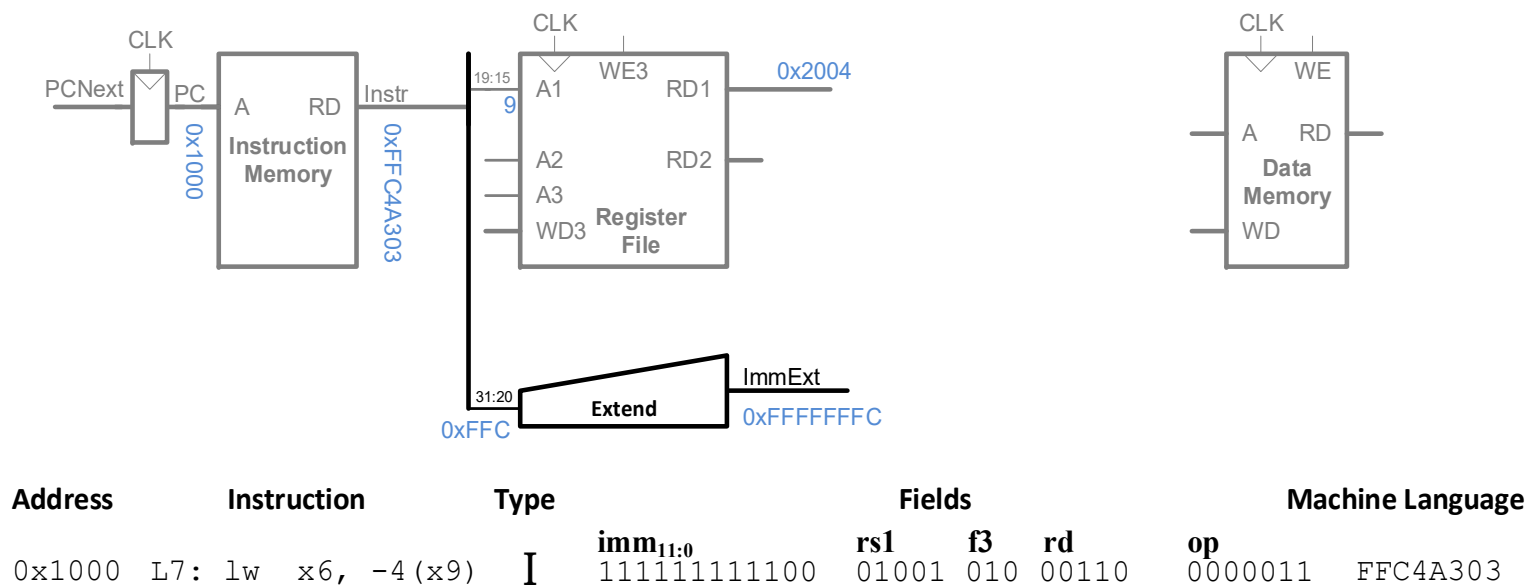
“Steps” are not necessarily sequential. Step 3 is concurrent with Step 2



Single-Cycle Datapath: lw Address

STEP 4: Compute the memory address


ALUControl _{2:0}	Function
000	add
001	subtract
010	and
011	or
101	SLT

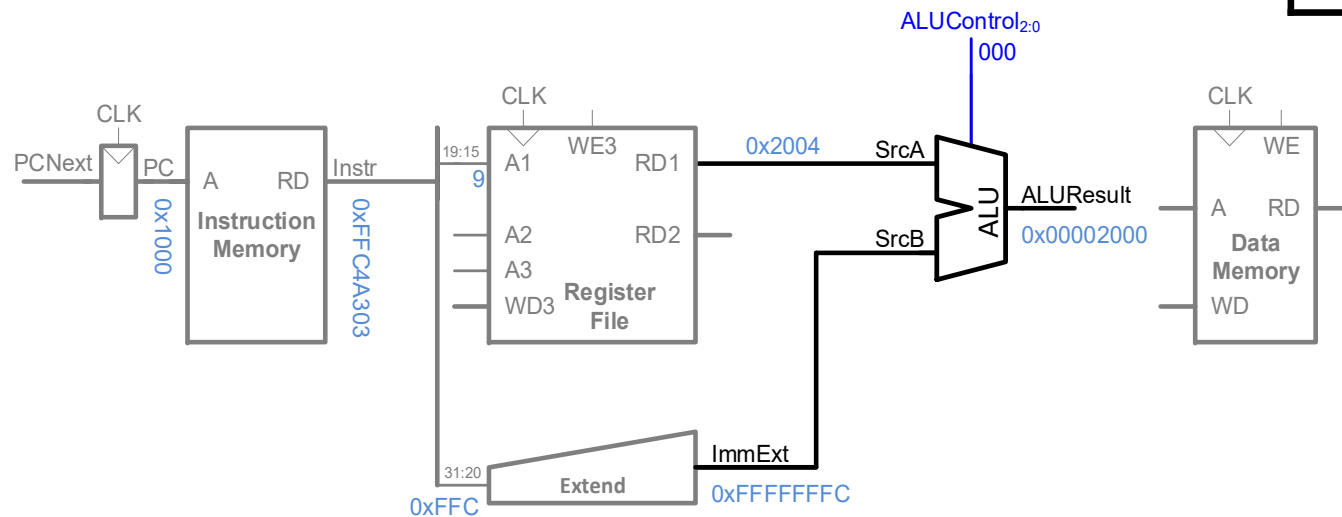

Address	Instruction	Type	Fields	Machine Language
0x1000	L7: lw x6, -4(x9)	I	<div> <div>imm_{11:0}</div> <div>111111111100</div> </div> <div> <div>rs1</div> <div>01001</div> </div> <div> <div>f3</div> <div>010</div> </div> <div> <div>rd</div> <div>00110</div> </div>	<div> <div>op</div> <div>0000011</div> </div> <div>FFC4A303</div>

Single-Cycle Datapath: lw Mem Read

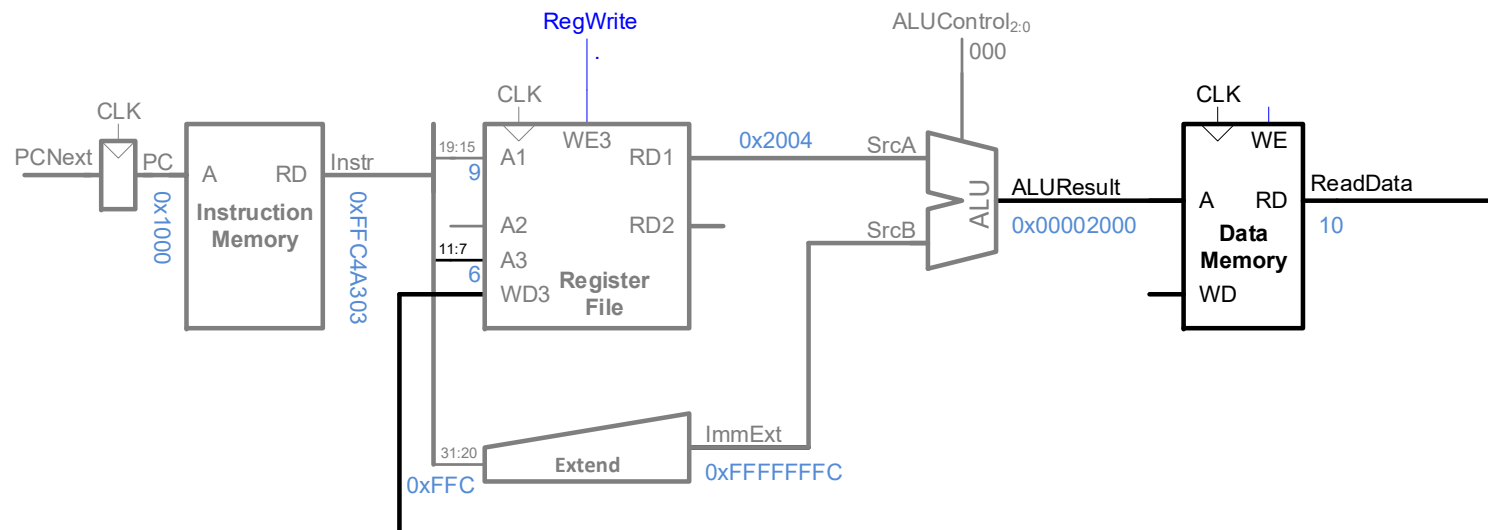STEP 5: Read data from memory and write it back to register file




Address	Instruction	Type	Fields				Machine Language	
0x1000	L7: lw x6, -4(x9)	I	imm _{11:0}	rs1	f3	rd	op	
			111111111100	01001	010	00110	0000011	FFC4A303

Single-Cycle Datapath: lw Increment

STEP 6: Determine address of next instruction

Step 6 is concurrent with other steps

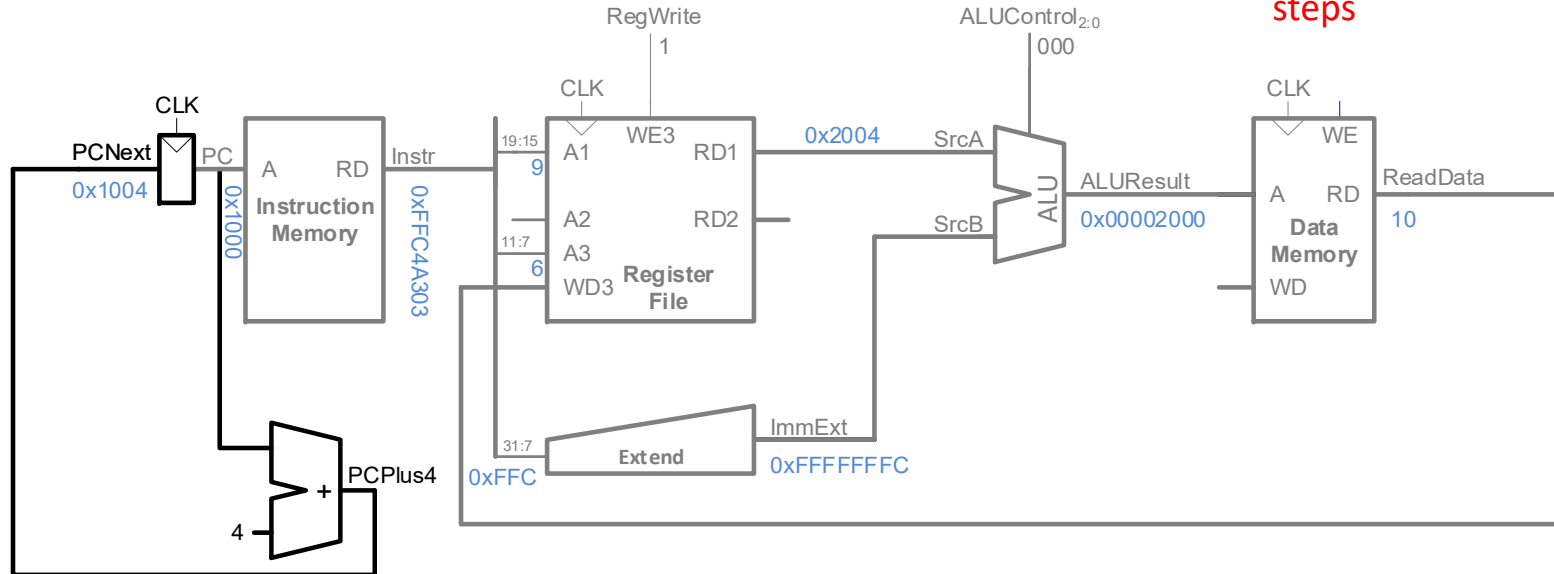

Address	Instruction	Type	Fields	Machine Language
0x1000	L7: lw x6, -4(x9)	I	$imm_{11:0}$ 111111111100 $rs1$ 01001 $f3$ 010 rd 00110 op 0000011	FFC4A303

Example Program

Let's extend the datapath to enable execution of other (core) instructions


Example Program:

Address	Instruction	Type	Fields					Machine Language	
0x1000	L7: lw x6, -4(x9)	I	imm _{11:0}	rs1	f3	rd	op		
			1111111111100	01001	010	00110	0000011	FFC4A303	
0x1004	sw x6, 8(x9)	S	imm _{11:5}	rs2	rs1	f3	imm _{4:0}	op	
			0000000	00110	01001	010	01000	0100011	0064A423
0x1008	or x4, x5, x6	R	funct7	rs2	rs1	f3	rd	op	
			0000000	00110	00101	110	00100	0110011	0062E233
0x100C	beq x4, x4, L7	B	imm _{12,10:5}	rs2	rs1	f3	imm _{4:1,11}	op	
			1111111	00100	00100	000	10101	1100011	FE420AE3

Single-Cycle Datapath: sw

- **Immediate:** now in {instr[31:25], instr[11:7]}
- **Add control signals:** ImmSrc, MemWrite

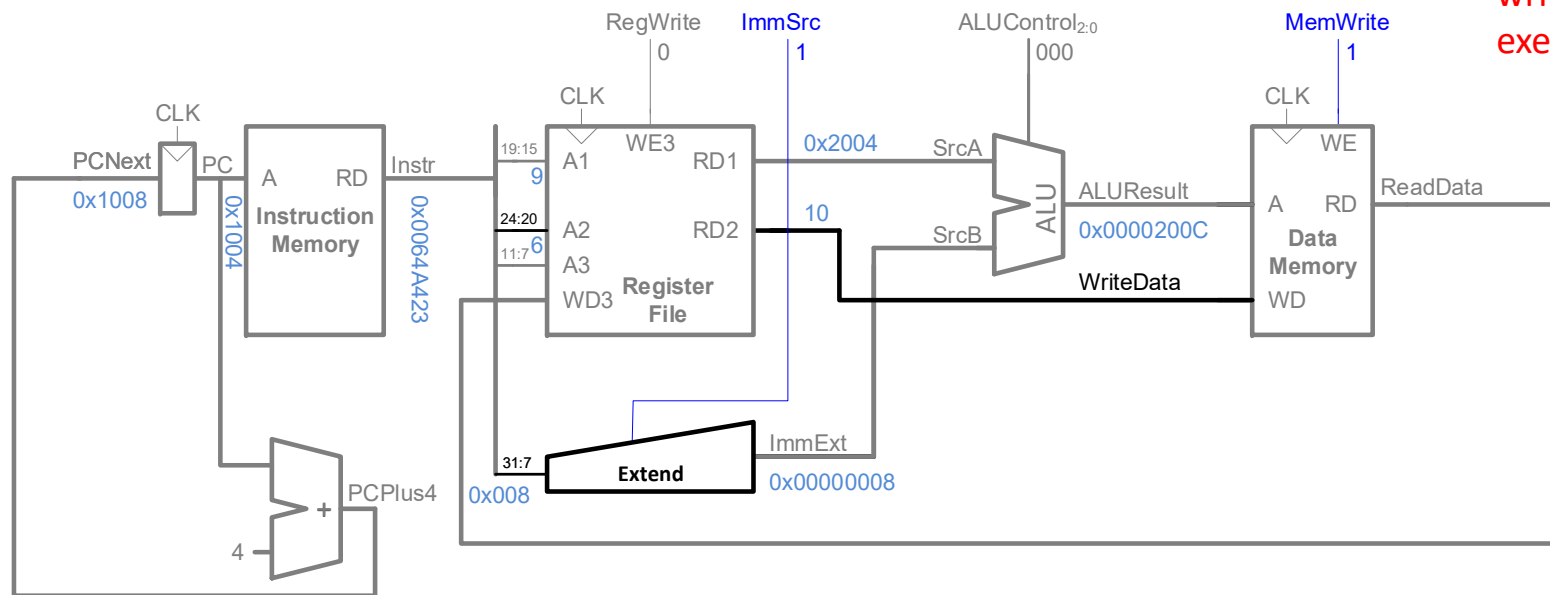- What is slower, RF or Extend unit?
- Is Rs2 read when executing lw? Is it written to memory? Is something written to RF when executing sw?




Address	Instruction	Type	Fields					Machine Language	
			imm _{11:5}	rs2	rs1	f3	imm _{4:0}	op	
0x1004	sw x6, 8(x9)	S	00000000	00110	01001	010	01000	0100011	0064A423


Single-Cycle Datapath: Immediate

ImmSrc	ImmExt	Instruction Type
0	{{20{instr[31]}}, instr[31:20] }	I-Type
1	{{20{instr[31]}}, instr[31:25], instr[11:7] }	S-Type

I-Type

 

S-Type

 


Single-Cycle Datapath: R-type

- What does the output of Extend unit represent?

- Same rs1, rs2, rd field positions help

- Read from **rs1** and **rs2** (instead of imm)
- Write *ALUResult* to **rd**

ALUControl _{2:0}	Function
000	add
001	subtract
010	and
011	or
101	SLT

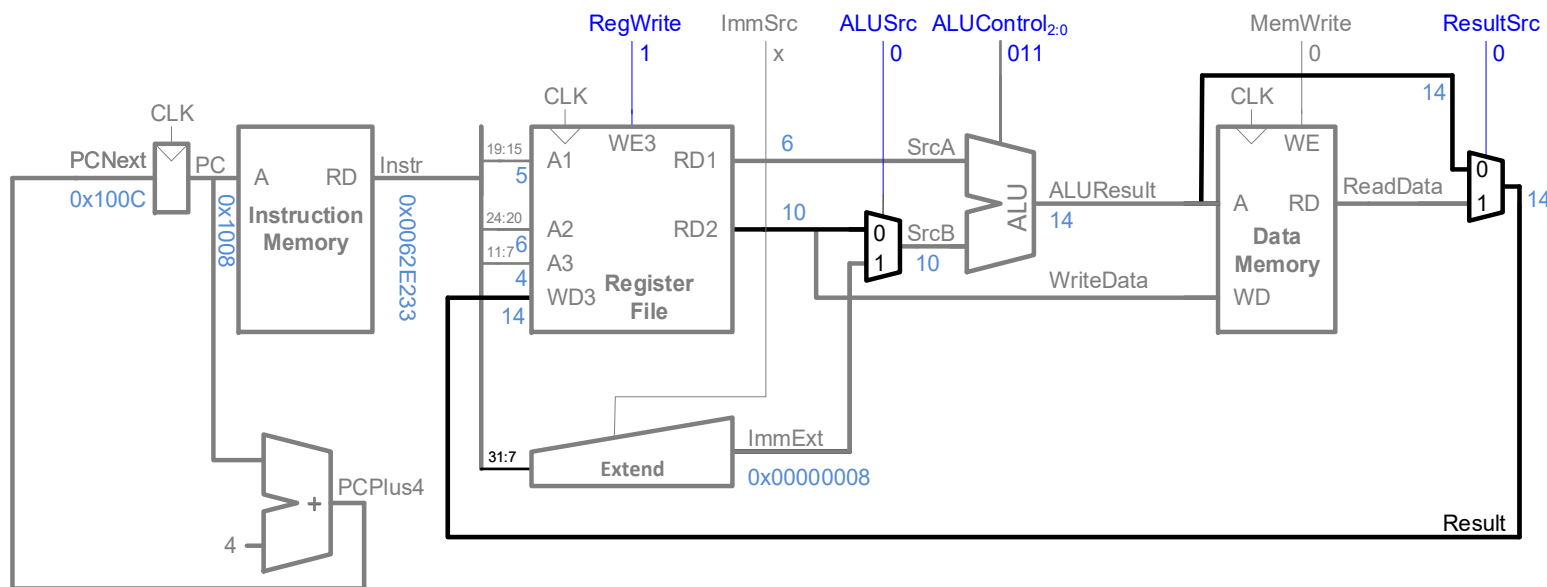


Address	Instruction	Type	Fields	Machine Language
0x1008	or x4, x5, x6	R	funct7 0000000	rs2 00110
			rs1 00101	f3 110
			rd 00100	op 0110011
				0062E233

Single-Cycle Datapath: beq

Calculate **target address**: $PCTarget = PC + ImmExt$

ALUControl _{2:0}	Function
000	add
001	subtract
010	and
011	or
101	SLT

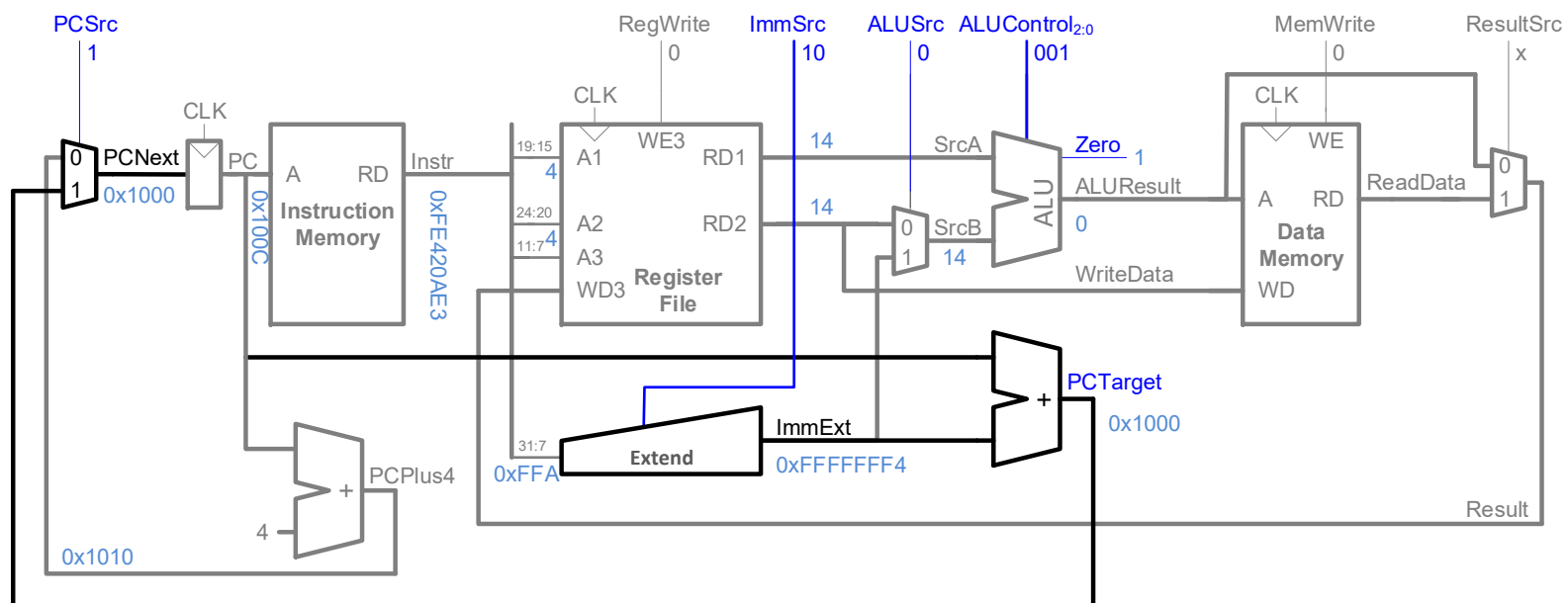


Address	Instruction	Type	Fields						Machine Language
0x100C	beq x4, x4, L7	B	imm _{12,10:5}	rs2	rs1	f3	imm _{4:1,11}	op	FE420AE3
			1111111	00100	00100	000	10101	1100011	


Single-Cycle Datapath: ImmExt

ImmSrc _{1:0}	ImmExt	Instruction Type
00	{{20{instr[31]}}, instr[31:20] }	I-Type
01	{{20{instr[31]}}, instr[31:25], instr[11:7] }	S-Type
10	{{19{instr[31]}}, instr[31], instr[7], instr[30:25], instr[11:8], 1'b0 }	B-Type


I-Type

 


S-Type

 

B-Type

 


Single-Cycle RISC-V Processor

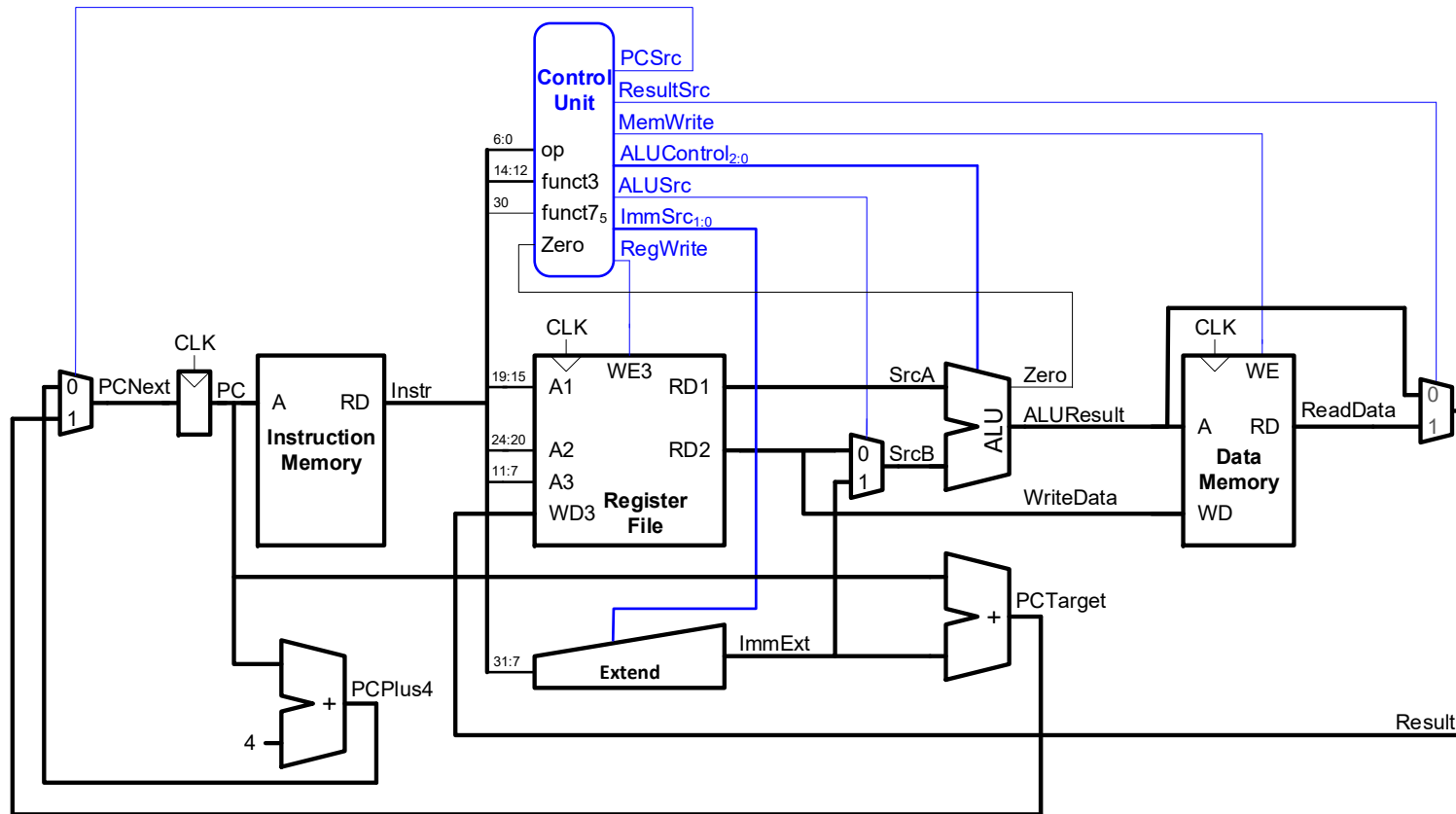


Single-Cycle Control

High-Level View

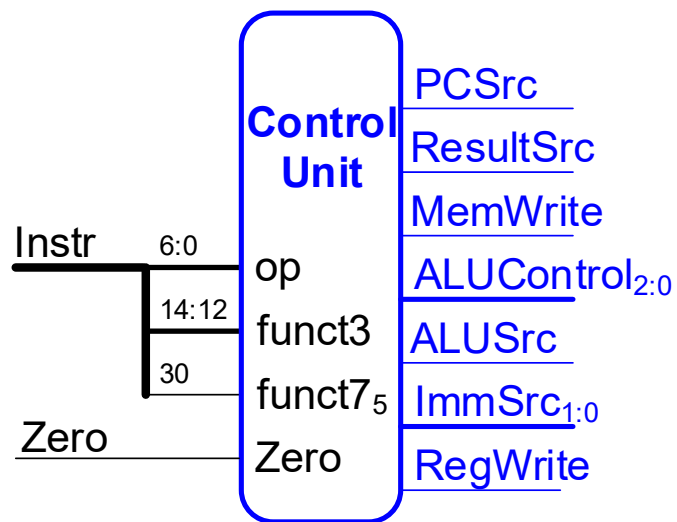


Low-Level View

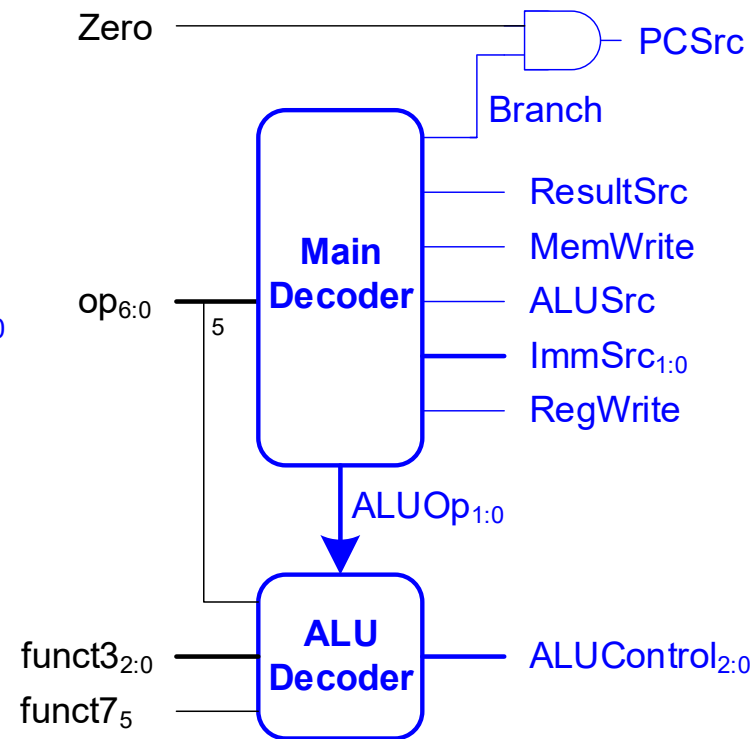


Single-Cycle Control: Main Decoder

op	Instr.	RegWrite	ImmSrc	ALUSrc	MemWrite	ResultSrc	Branch	ALUOp
3	lw							
35	sw							
51	R-type							
99	beq							

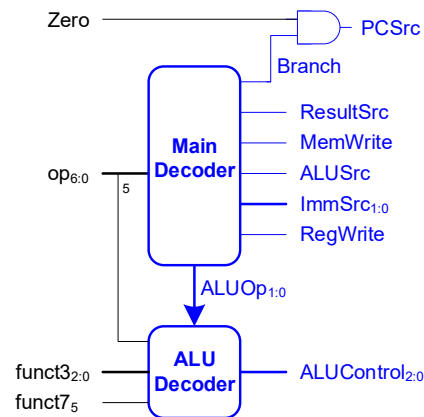


Review: ALU

ALUControl _{2:0}	Function
000	add
001	subtract
010	and
011	or
101	SLT

 


Review: ALU

ALUControl _{2:0}	Function
000	add
001	subtract
010	and
011	or
101	SLT

 


Single-Cycle Control: ALU Decoder

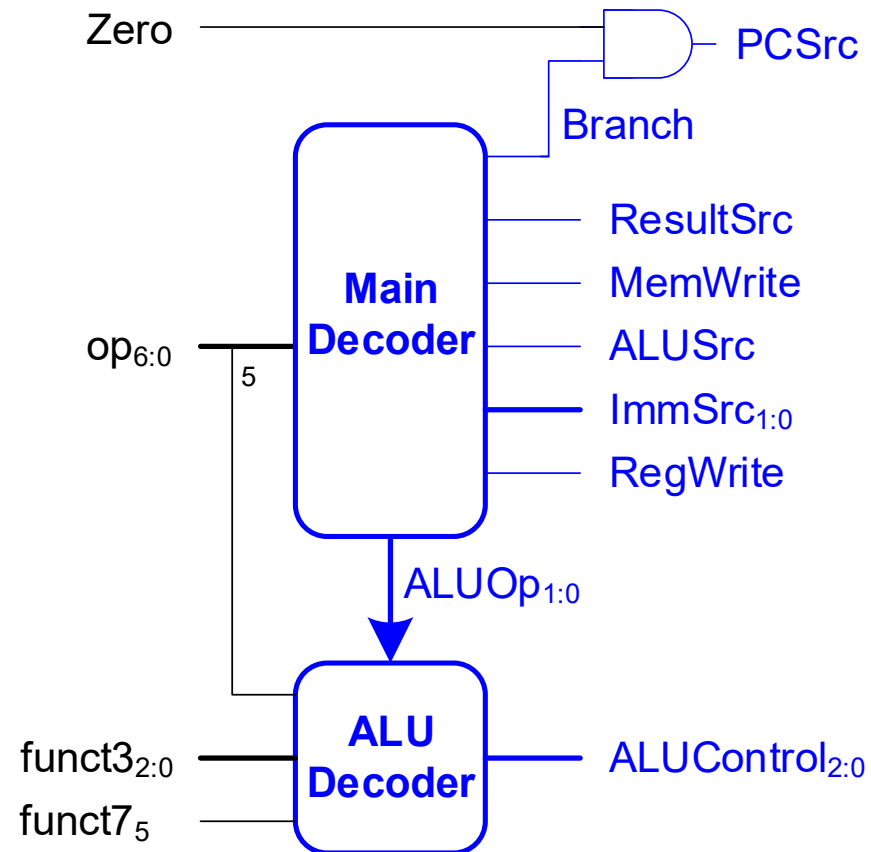


Single-Cycle Control: ALU Decoder

ALUOp	funct3	op ₅ , funct7 ₅	Instruction	ALUControl _{2:0}
00	x	x	lw, sw	000 (add)
01	x	x	beq	001 (subtract)
10	000	00, 01, 10	add	000 (add)
	000	11	sub	001 (subtract)
	010	x	slt	101 (set less than)
	110	x	or	011 (or)
	111	x	slt	010 (and)

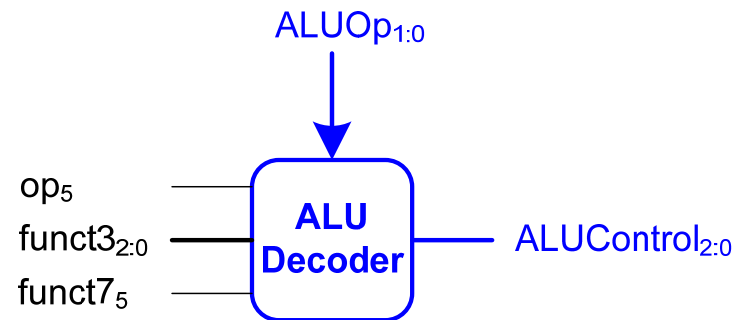

Example: and

op	Instruct	RegWrite	ImmSrc	ALUSrc	MemWrite	ResultSrc	Branch	ALUOp
51	R-type	1	XX	0	0	0	0	10

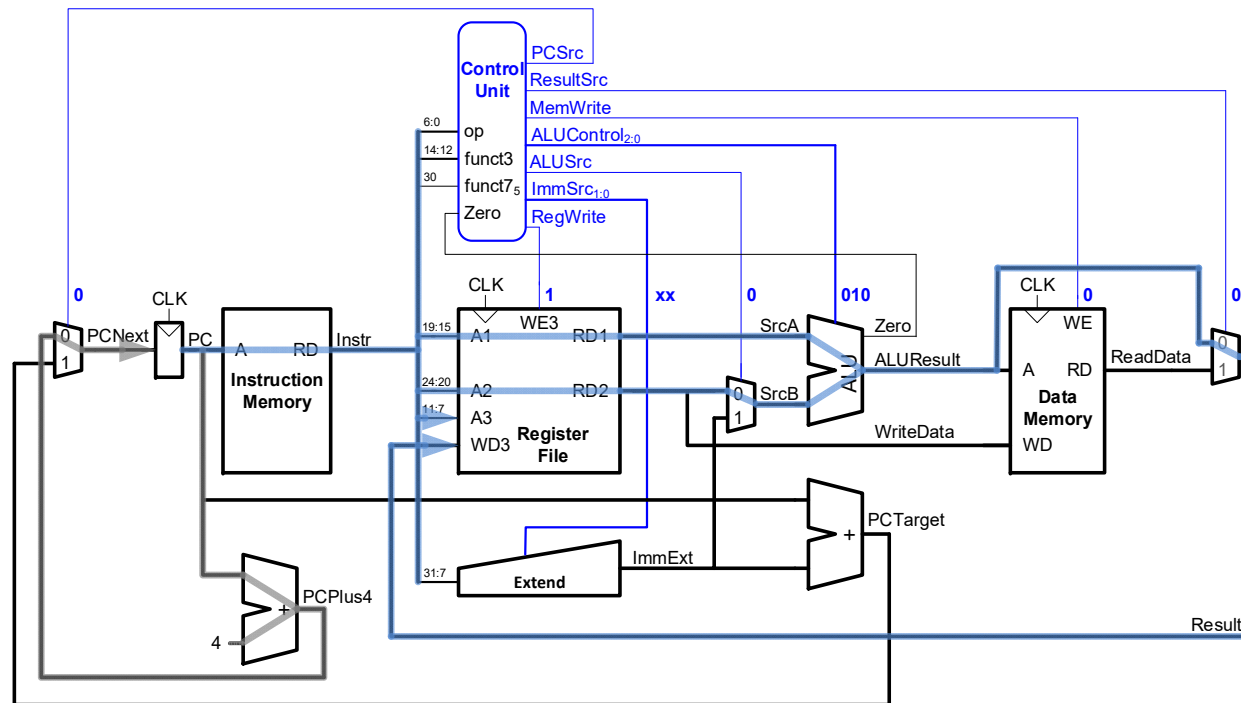

and x5, x6, x7

Extended Functionality: I-Type ALU

Enhance the single-cycle processor to handle **I-Type ALU instructions**: `addi`, `andi`, `ori`, and `slti`


- **Similar to R-type** instructions
- But **second source** comes from **immediate**
- Change ***ALUSrc*** to select the immediate
- And ***ImmSrc*** to pick the correct immediate

Extended Functionality: I-Type ALU

op	Instruct.	RegWrite	ImmSrc	ALUSrc	MemWrite	ResultSrc	Branch	ALUOp
3	lw	1	00	1	0	1	0	00
35	sw	0	01	1	1	X	0	00
51	R-type	1	XX	0	0	0	0	10
99	beq	0	10	0	0	X	1	01
19	I-type	1	00	1	0	0	0	10

Extended Functionality: addi

op	Instruct.	RegWrite	ImmSrc	ALUSrc	MemWrite	ResultSrc	Branch	ALUOp
19	I-type	1	00	1	0	0	0	10

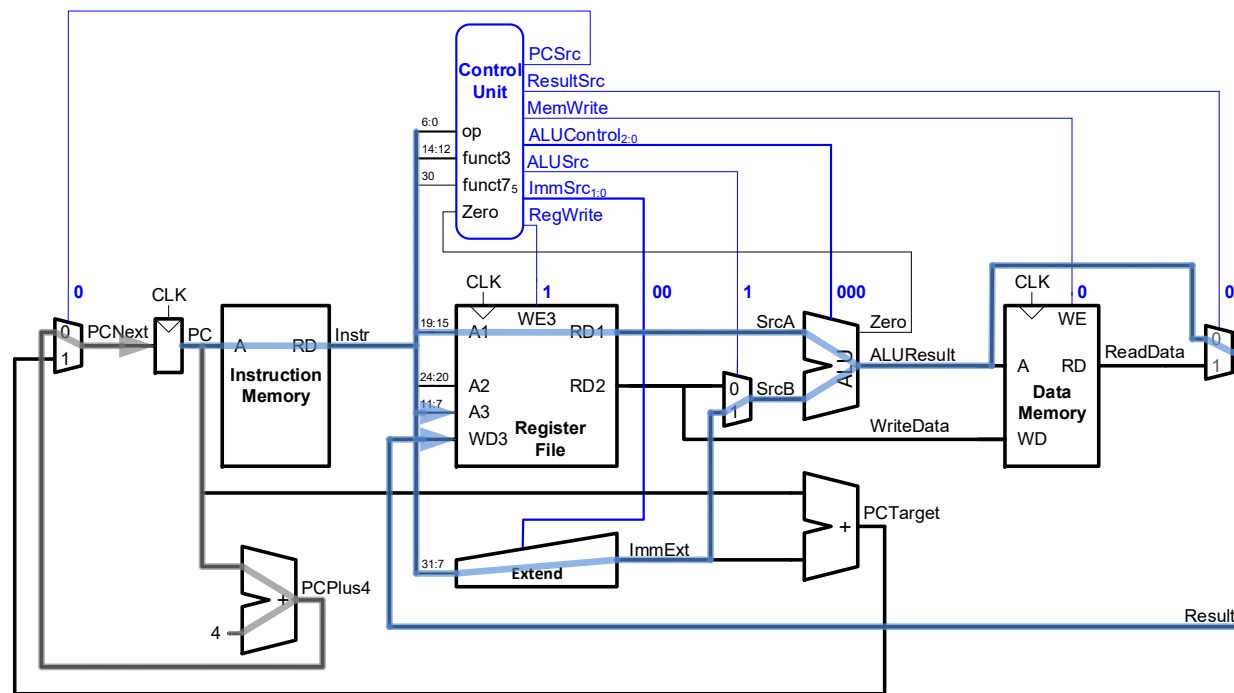


`addi x5, x6, -33`

Extended Functionality: jal

Enhance the single-cycle processor to handle `jal`

- **Similar to beq**
- But jump is **always taken**
 - *PCSrc* should be 1
- **Immediate format** is different
 - Need a new *ImmSrc* of 11
- And `jal` must **compute PC+4** and **store in rd**
 - Take PC+4 from adder through ResultMux


Extended Functionality: jal

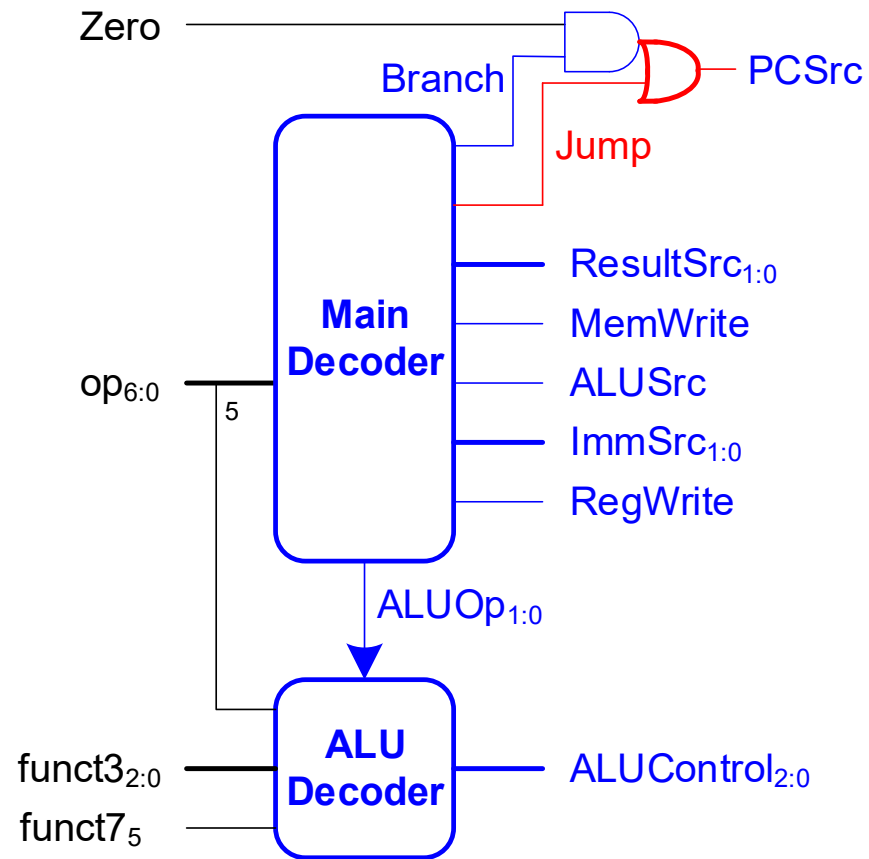


Extended Functionality: ImmExt

ImmSrc _{1:0}	ImmExt	Instruction Type
00	{{20{instr[31]}}, instr[31:20]}	I-Type
01	{{20{instr[31]}}, instr[31:25], instr[11:7]}	S-Type
10	{{19{instr[31]}}, instr[31], instr[7], instr[30:25], instr[11:8], 1'b0}	B-Type
11	{{12{instr[31]}}, instr[19:12], instr[20], instr[30:21], 1'b0 }	J-Type


I-Type

 


B-Type

 

S-Type

 

J-Type

 


Extended Functionality: jal

op	Instruct.	RegWrite	ImmSrc	ALUSrc	MemWrite	ResultSrc	Branch	ALUOp	Jump
3	lw	1	00	1	0	01	0	00	0
35	sw	0	01	1	1	XX	0	00	0
51	R-type	1	XX	0	0	00	0	10	0
99	beq	0	10	0	0	XX	1	01	0
19	l-type	1	00	1	0	00	0	10	0
111	jal	1	11	X	0	10	X	XX	1

Extended Functionality: jal

op	Instruct.	RegWrite	ImmSrc	ALUSrc	MemWrite	ResultSrc	Branch	ALUOp	Jump
111	jal	1	11	X	0	10	X	XX	1

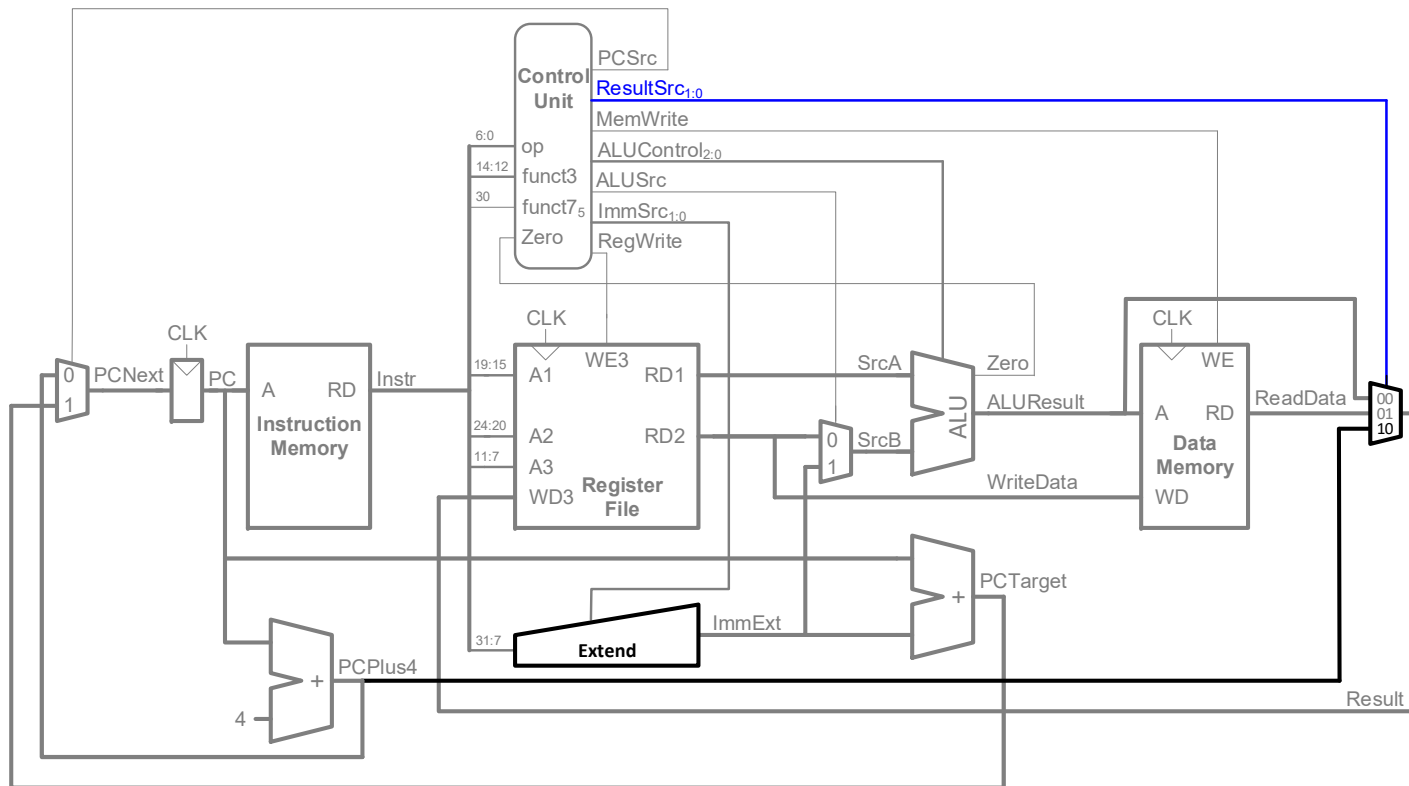


Processor Performance

Program Execution Time

$$= (\text{\#instructions})(\text{cycles/instruction})(\text{seconds/cycle})$$

$$= \text{\# instructions} \times \text{CPI} \times T_C$$

Single-Cycle Processor Performance

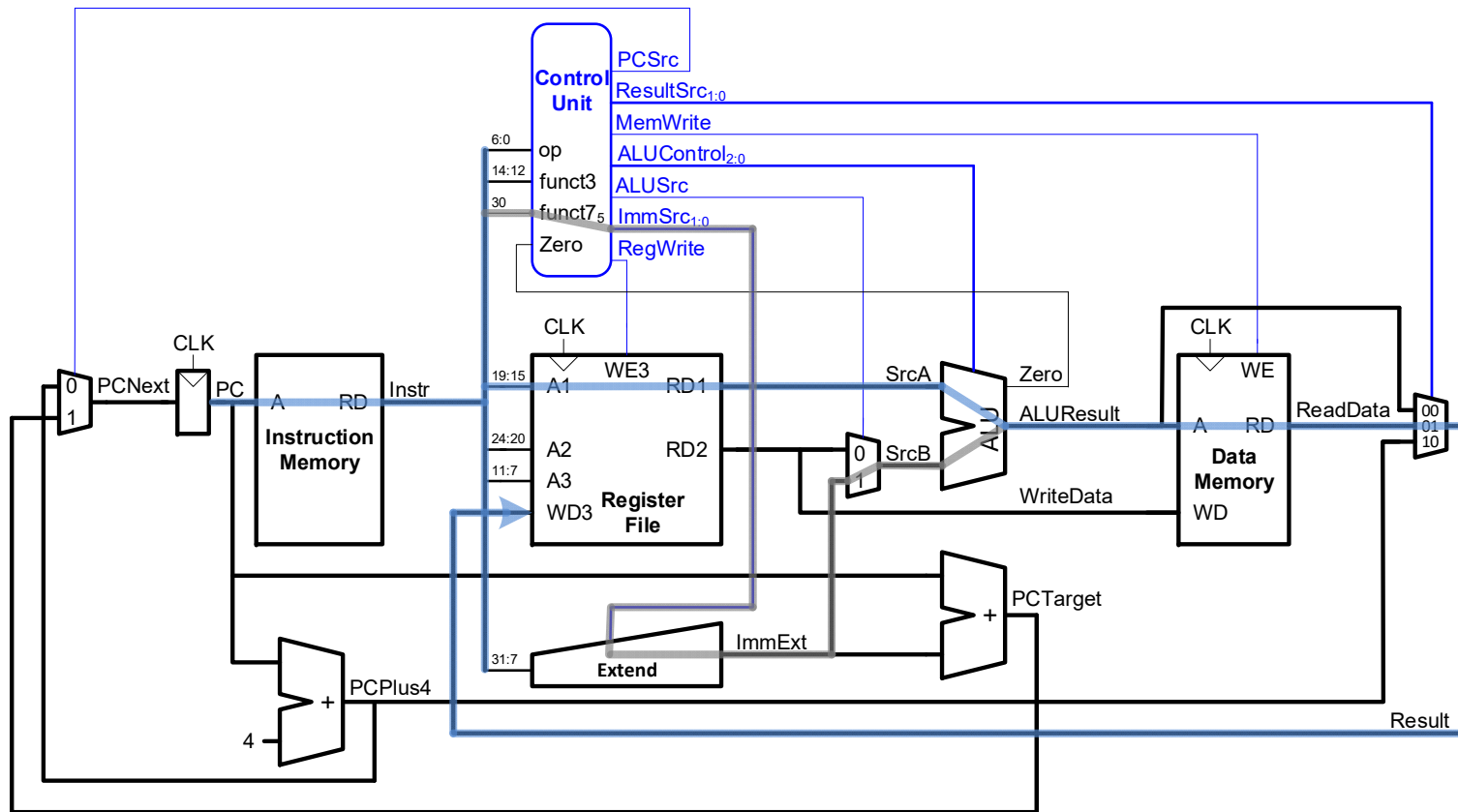

T_C limited by critical path (1w)

Single-Cycle Processor Performance

- Single-cycle critical path:


$$T_{c_single} = t_{pcq_PC} + t_{mem} + \max[t_{RFread}, t_{dec} + t_{ext} + t_{mux}] + t_{ALU} + t_{mem} + t_{mux} + t_{RFsetup}$$

- Typically, limiting paths are:

- memory, ALU, register file

- So,
$$\begin{aligned} T_{c_single} &= t_{pcq_PC} + t_{mem} + t_{RFread} + t_{ALU} + t_{mem} + t_{mux} + t_{RFsetup} \\ &= t_{pcq_PC} + 2t_{mem} + t_{RFread} + t_{ALU} + t_{mux} + t_{RFsetup} \end{aligned}$$

Timing for LW Instruction

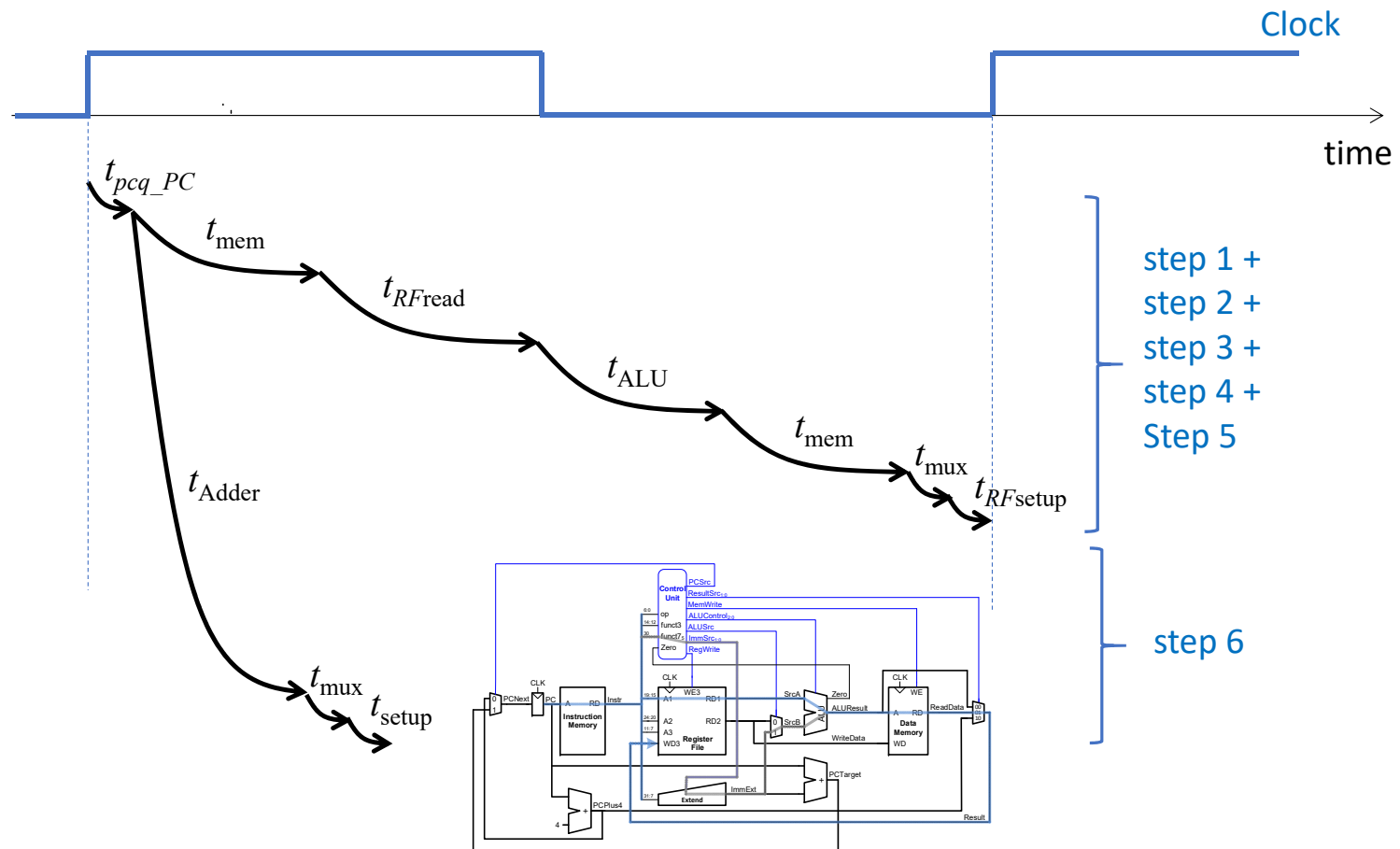

Single-Cycle Processor Performance

Element	Parameter	Delay (ps)
Register clock-to-Q	t_{pcq_PC}	40
Register setup	t_{setup}	50
Multiplexer	t_{mux}	30
AND-OR gate	t_{AND-OR}	20
ALU	t_{ALU}	120
Decoder (Control Unit)	t_{dec}	25
Extend unit	t_{ext}	35
Memory read	t_{mem}	200
Register file read	t_{RFread}	100
Register file setup	$t_{RFsetup}$	60

$$T_{c_single} = t_{pcq_PC} + 2t_{mem} + t_{RFread} + t_{ALU} + t_{mux} + t_{RFsetup}$$

$$=$$

Single-Cycle Processor Example

Program with 100 billion instructions:

$$\text{Execution Time} = \# \text{ instructions} \times \text{CPI} \times T_C$$