

# Lab 4 Report

## Number of hours spent on lab

I spent about 16 hours on this lab.

Table 1

Cycle	reset	PC	Instr	SrcA	SrcB	ALUResult	Zero	PCSrc	WriteData	MemWrite	Read Data	RegWrite	ImmSrc	ImmExt	PCTarget
1	1	00	addi x2, x0, 5	0	5	5	0	0	x	0	x	1	000	5	x
2	0	04	addi x3, x0, 12	0	c	c	0	0	x	0	x	1	000	c	x
3	0	08	addi x7, x3, -9	c	-9	3	0	0	x	0	x	1	000	-9	x
4	0	0C	or x4, x7, x2	3	5	7	0	0	x	0	x	1	x	x	x
5	0	10	and x5, x3, x4	c	7	4	0	0	x	0	x	1	x	x	x
6	0	14	add x5, x5, x4	4	7	b	0	0	x	0	x	1	x	x	x
7	0	18	beq x5, x7, end	b	3	8	0	0	x	0	x	0	010	0x30	0x48
8	0	1C	slt x4, x3, x4	c	7	0	1	0	x	0	x	1	x	x	x
9	0	20	beq x4, x0, around	0	0	0	1	1	x	0	x	0	010	8	0x28
10	0	28	slt x4, x7, x2	3	5	1	0	0	x	0	x	1	x	x	x
11	0	2C	add x7, x4, x5	1	b	c	0	0	x	0	x	1	x	x	x
12	0	30	sub x7, x7, x2	c	5	7	0	0	x	0	x	1	x	x	x
13	0	34	sw x7, 84(x3)	c	0x54	0x60	0	0	7	1	x	0	001	0x54	x
14	0	38	lw x2, 96(x0)	0	0x60	0x60	0	0	x	0	7	1	000	0x60	x
15	0	3C	add x9, x2, x5	7	b	0x12	0	0	x	0	x	1	x	x	x
16	0	40	jal x3, end	x	x	x	x	1	x	0	x	1	011	8	0x48
17	0	48	add x2, x2, x9	7	0x12	0x19	0	0	x	0	x	1	x	x	x
18	0	4C	sw x2, 0x20(x3)	0x44	0x20	0x64	0	0	0x19	1	x	0	001	0x20	x
19	0	50	lui x2, 0x0BEEF	x	x	x	x	0	x	0	x	1	100	0x0beef000	x
20	0	54	sw x2, 0x24(x3)	0x44	0x24	0x68	0	0	0x0beef000	1	x	0	001	0x24	x
21	0	58	beq x2, x2, done	0x0beef000	0x0beef000	0	1	0	x	0	x	0	010	0	0x58

## Simulation Waveforms


 


Table 2

op	Instruct.	RegWrite	ImmSrc	ALUSrc	MemWrite	ResultSrc	Branch	ALUOp	Jump
3	lw	1	000	1	0	01	0	00	0
35	sw	0	001	1	1	XX	0	00	0
51	R-type	1	XXX	0	0	00	0	10	0
99	beq	0	010	0	0	XX	1	01	0
19	I-type	1	000	1	0	00	0	10	0
111	jal	1	011	X	0	10	0	XX	1
55	lui	1	100	X	0	11	0	XX	0

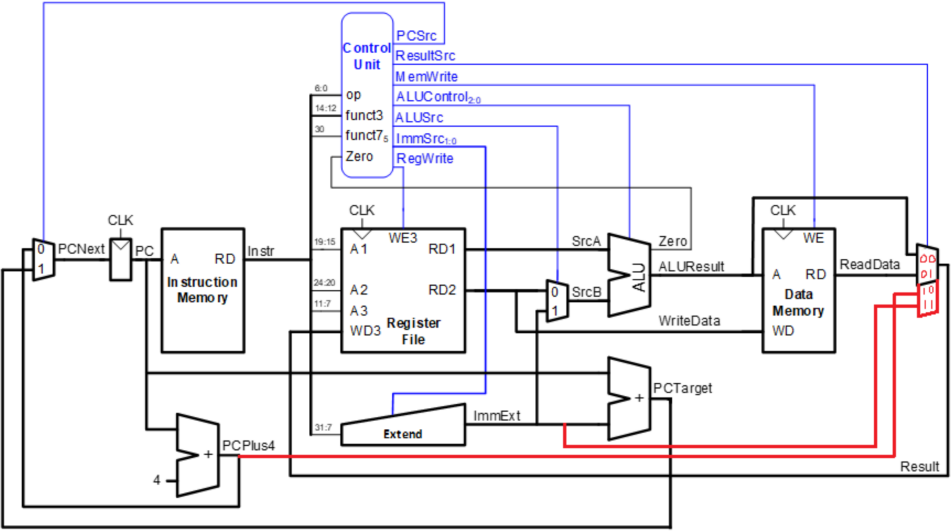

ucsbece154a\_controller.v

```
// ucsbece154a_controller.v
// All Rights Reserved
// Copyright (c) 2023 UCSB ECE
// Distribution Prohibited
```

```
module ucsbece154a_controller (
    input      [6:0] op_i,
    input      [2:0] funct3_i,
```

```

    input          funct7b5_i,
    input          zero_i,
    output wire     RegWrite_o,
    output wire     ALUSrc_o,
    output wire     MemWrite_o,
    output wire     [1:0] ResultSrc_o,
    output reg      [2:0] ALUControl_o,
    output wire     PCSrc_o,
    output wire     [2:0] ImmSrc_o
);

`include "ucsbece154a_defines.vh"

// TO DO: Generate properly PCSrc by replacing all `z` values with the correct values

wire branch, jump;
assign PCSrc_o = (zero_i & branch) | jump;

// TO DO: Implement main decoder
// • Replace all `z` values with the correct values
// • Extend the code to implement jal and lui

reg [11:0] controls;
wire [1:0] ALUOp;

assign {RegWrite_o,
        ImmSrc_o,
        ALUSrc_o,
        MemWrite_o,
        ResultSrc_o,
        branch,
        ALUOp,
        jump} = controls;

always @ * begin
    case (op_i)
        instr_lw_op:      controls = 12'b100010010000;
        instr_sw_op:      controls = 12'b000111000000;
        instr_Rtype_op:   controls = 12'b100000000100;
        instr_beq_op:     controls = 12'b001000001010;
        instr_ItypeALU_op: controls = 12'b100010000100;
        instr_jal_op:     controls = 12'b101100100001;
        instr_lui_op:     controls = 12'b110000110000;

        default: begin
            controls = 12'b000000000000;
            `ifdef SIM
                $warning("Unsupported op given: %h", op_i);
            `else
                ;
            `endif
        end
    endcase
end

// TO DO: Implement ALU decoder by replacing all `z` values with the correct values

wire RtypeSub;

assign RtypeSub = funct7b5_i & op_i[5];

always @ * begin
    case(ALUOp)
        ALUOp_mem:        ALUControl_o = 3'b000;
        ALUOp_beq:        ALUControl_o = 3'b001;
        ALUOp_other:
            case(funct3_i)
                instr_addsub_func3:
                    if(RtypeSub) ALUControl_o = 3'b001;
                    else        ALUControl_o = 3'b000;
                instr_slt_func3:  ALUControl_o = 3'b101;
                instr_or_func3:   ALUControl_o = 3'b011;
            endcase
    endcase
end

```

```
instr_and_func3:  ALUControl_o = 3'b010;
default: begin
    ALUControl_o = 3'b000;
    `ifdef SIM
        $warning("Unsupported funct3 given: %h", funct3_i);
    `else
        ;
    `endif
end
endcase
default:
    `ifdef SIM
        $warning("Unsupported ALUOp given: %h", ALUOp);
    `else
        ;
    `endif
endcase
end

endmodule
```

ucsbece154a\_datapath.v

```
// ucsbece154a_datapath.v
// All Rights Reserved
// Copyright (c) 2023 UCSB ECE
// Distribution Prohibited

module ucsbece154a_datapath (
    input          clk, reset,
    input          RegWrite_i,
    input          [2:0] ImmSrc_i,
    input          ALUSrc_i,
    input          PCSrc_i,
    input          [1:0] ResultSrc_i,
    input          [2:0] ALUControl_i,
    output         zero_o,
    output reg     [31:0] pc_o,
    input          [31:0] instr_i,
    output wire    [31:0] aluresult_o, writedata_o,
    input          [31:0] readdata_i
);

`include "ucsbece154a_defines.vh"

/// Your code here

wire [31:0] PCNext, PCPlus4, PCTarget;
reg  [31:0] ImmExt;
wire [31:0] SrcA, SrcB;
reg  [31:0] Result;
wire dummy1;
wire dummy2;
assign PCNext = PCSrc_i ? PCTarget : PCPlus4;
assign SrcB = ALUSrc_i ? ImmExt : writedata_o;

always @ * begin
    case (ResultSrc_i)
        2'b00: Result = aluresult_o;
        2'b01: Result = readdata_i;2'b10: Result = PCPlus4;
        2'b11: Result = ImmExt;
        default: Result = 32'b0;
    endcase
end

always @ * begin
    case (ImmSrc_i)
        3'b000: ImmExt = {{20{instr_i[31]}}, instr_i[31:20]};
        3'b001: ImmExt = {{20{instr_i[31]}}, instr_i[31:25], instr_i[11:7]};
        3'b010: ImmExt = {{20{instr_i[31]}}, instr_i[7], instr_i[30:25], instr_i[11:8], 1'b0};
        3'b011: ImmExt = {{12{instr_i[31]}},instr_i[19:12],instr_i[20],instr_i[30:21],1'b0};
        3'b100: ImmExt = {instr_i[31:12],12'b0};
        default: ImmExt = 32'b0;
    endcase
end
```

```
        endcase
    end

    always @(posedge clk or posedge reset) begin
        if (reset) begin
            pc_o <= 32'b0;
        end
        else begin
            pc_o <= PCNext;
        end
    end

    assign PCPlus4 = pc_o + 32'b100;
    assign PCTarget = pc_o + ImmExt;

    ucsbece154a_alu ALU (
        .a_i(SrcA),
        .b_i(SrcB),
        .alucontrol_i(ALUControl_i),
        .result_o(alureresult_o),
        .zero_o(zero_o)
    );

    ucsbece154a_rf rf(
        .clk(clk),
        .a1_i(instr_i[19:15]),
        .a2_i(instr_i[24:20]),
        .a3_i(instr_i[11:7]),
        .rd1_o(SrcA),
        .rd2_o(writedata_o),
        .we3_i(RegWrite_i),
        .wd3_i(Result)
    );

endmodule
```