

Digital Building Blocks: Adders

Acknowledgment: Slides are adapted from Harris and Harris
and Hennessy and Patterson textbooks

Introduction

- **Digital building blocks:**

- Gates, multiplexers, decoders, registers, arithmetic circuits, counters, memory arrays, logic arrays

- **Building blocks demonstrate hierarchy, modularity, and regularity:**

- Hierarchy of simpler components
- Well-defined interfaces and functions
- Regular structure easily extends to different sizes

1-Bit Adder

Any fan-in gates:

$$t_{C_{out}} = t_{AND2} + t_{OR3}$$

$$t_S = t_{XOR3}$$

$$A_{FA} = 3A_{AND2} + A_{OR3} + A_{XOR3}$$

Only fan-in two gates:


$$t_{C_{out}} = t_{AND2} + 2t_{OR2}$$

$$t_S = 2t_{XOR2}$$

$$A_{FA} = 3A_{AND2} + 2A_{OR2} + 2A_{XOR2}$$

**Full
Adder**

Cin = 0 for
“half adder”

 

| C _{in} | A | B | C _{out} | S |
|-----------------|---|---|------------------|---|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 1 | 1 |


$$S = A \oplus B \oplus C_{in}$$

$$C_{out} = AB + AC_{in} + BC_{in}$$

Multibit Adders (CPAs)


- Types of carry propagate adders (CPAs):
 - Ripple-carry (slow)
 - Carry-lookahead (fast)
 - Prefix (faster)
- Carry-lookahead & prefix adders faster for large adders but require more hardware

Symbol

 

Ripple-Carry Adder

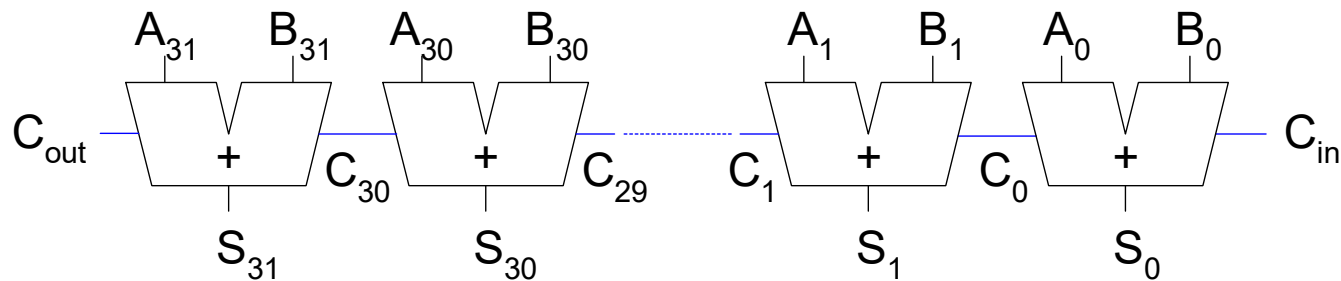- Chain 1-bit adders together
- Carry ripples through entire chain
- Disadvantage: **slow**



Ripple-Carry Adder Delay and Complexity

$$A_{\text{ripple}} = NA_{FA}$$


where A_{FA} is the area of a 1-bit full adder

$$t_{\text{ripple}} = Nt_{FA}$$

where t_{FA} is the delay of a 1-bit full adder

- This is a crude estimation in terms of delays and complexity of subblocks. Sometimes (e.g. for clock cycle calculation) more accurate estimates are needed.

Ripple-Carry Adder (More Accurate) Delay

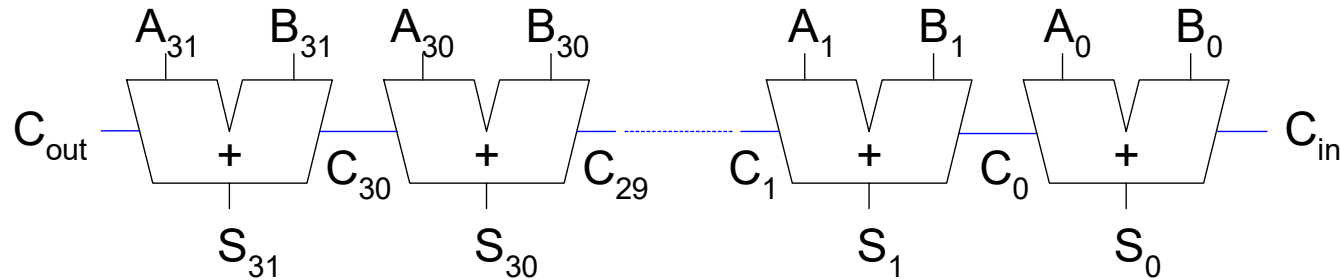

$t_{\text{AND2}} = t_{\text{OR2}} = 1 \text{ ns}$, $t_{\text{XOR2}} = 2 \text{ ns}$ only fan-in-two gates

$C_0 = A_0 B_0 + A_0 C_{\text{in}} + B_0 C_{\text{in}}$ takes 3 ns


$C_1 = A_1 B_1 + A_1 C_0 + B_1 C_0$ takes 6 ns

$S_{31} = 31 * 3 \text{ ns} + 4 \text{ ns} = 97 \text{ ns}$ (not accurate)

$S_{31} = 31 * 3 \text{ ns} + \underline{2 \text{ ns}} = \underline{95 \text{ ns}}$ (considering overlap)

$C_{\text{out}} = 31 * 3 \text{ ns} = 96 \text{ ns} \rightarrow \text{critical path}$

 A Better (FA) Design for Ripple-Carry Adder



$t_{\text{AND2}} = t_{\text{OR2}} = 1 \text{ ns}$, $t_{\text{XOR2}} = 2 \text{ ns}$ only fan-in-two gates


$C_0 = A_0 B_0 + (A_0 + B_0) C_{\text{in}}$ takes 3 ns

$C_1 = A_1 B_1 + (A_1 + B_1) C_0$ takes 5 ns

$S_{31} = C_{\text{out}} = 3 \text{ ns} + 30 * 2 \text{ ns} + 2 \text{ ns} = 65 \text{ ns}$

- Big idea here is to manipulate Boolean formulas and compute subexpressions as soon as Boolean variables are available. The same idea will be used for faster adders

A Hint on What Can be Improved Further

 

$t_{\text{AND2}} = t_{\text{OR2}} = 1 \text{ ns}$, $t_{\text{XOR2}} = 2 \text{ ns}$ only fan-in-two gates

$C_0 = A_0 B_0 + (A_0 + B_0) C_{\text{in}}$ takes 3 ns

$C_1 = A_1 B_1 + (A_1 + B_1) C_0$ takes 5 ns

Plug C_0 into the expression for C_1

$$\begin{aligned} C_1 &= A_1 B_1 + (A_1 + B_1) (A_0 B_0 + (A_0 + B_0) C_{\text{in}}) = \\ &= A_1 B_1 + (A_1 + B_1) (A_0 B_0) + (A_1 + B_1) (A_0 + B_0) C_{\text{in}} \end{aligned}$$

now takes 1 ns + 1 ns + 1 ns + 1 ns = 4 ns

Carry-Lookahead Adder

- Compute carry out (C_{out}) for k -bit blocks using *generate* and *propagate* signals
- **Some definitions:**
 - Column i produces a carry out by either *generating* a carry out or *propagating* a carry in to the carry out
 - Generate (G_i) and propagate (P_i) signals for each column:
 - Column i will generate a carry out if A_i AND B_i are both 1.

$$G_i = A_i B_i$$

- Column i will propagate a carry in to the carry out if A_i OR B_i is 1.

$$P_i = A_i + B_i$$

- The carry out of column i (C_i) is:

$$C_i = A_i B_i + (A_i + B_i) C_{i-1} = G_i + P_i C_{i-1}$$

Carry-Lookahead Addition

- **Step 1:** Compute G_i and P_i for all columns
- **Step 2:** Compute G and P for k -bit blocks
- **Step 3:** C_{in} propagates through each k -bit propagate/generate block

- **Example:** 4-bit blocks ($G_{3:0}$ and $P_{3:0}$) :

$$G_{3:0} = G_3 + P_3 (G_2 + P_2 (G_1 + P_1 G_0))$$

$$P_{3:0} = P_3 P_2 P_1 P_0$$



- **Generally,**


$$G_{i:j} = G_i + P_i (G_{i-1} + P_{i-1} (G_{i-2} + P_{i-2} G_j))$$

$$P_{i:j} = P_i P_{i-1} P_{i-2} P_j$$




$$C_i = G_{i:j} + P_{i:j} C_{j-1}$$

32-bit CLA with 4-bit Blocks

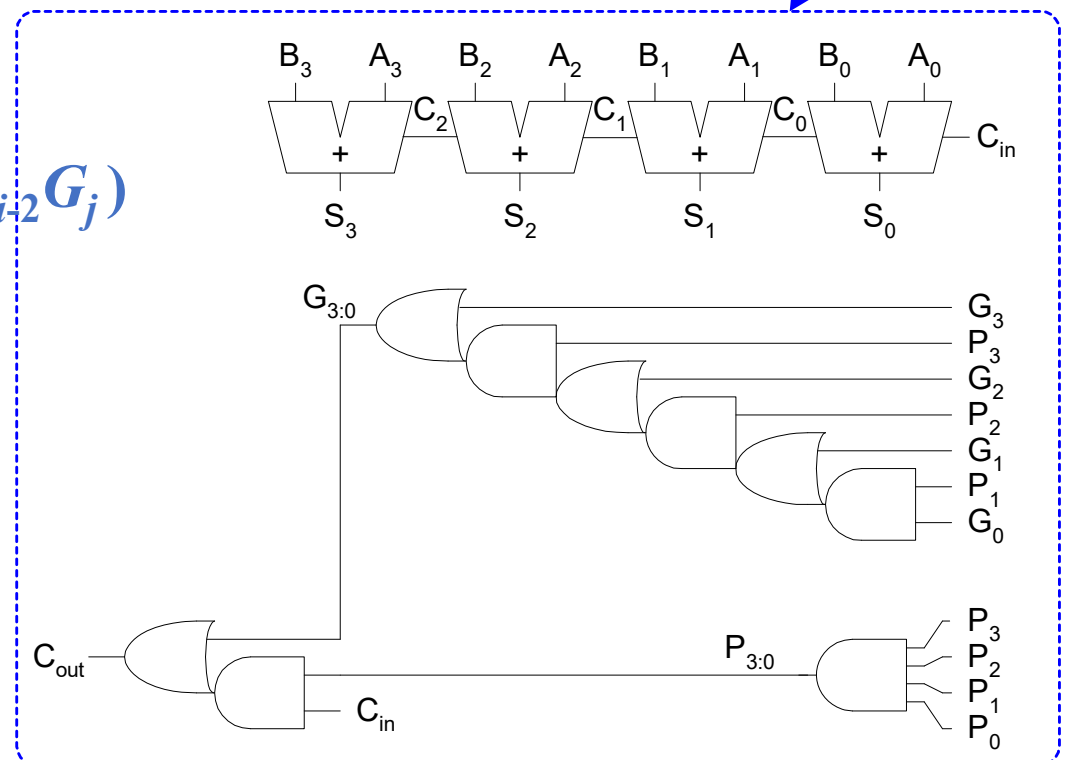 

 

Ripple-Carry

   

Carry-Lookahead

Carry-Lookahead Adder (Crude) Delay

For N -bit CLA with k -bit blocks:

$$t_{CLA} = t_{pg} + t_{pg_block} + (N/k - 1)t_{AND_OR} + kt_{FA}$$

- t_{pg} : delay to generate all P_i, G_i
- t_{pg_block} : delay to generate all $P_{i:j}, G_{i:j}$
- t_{AND_OR} : delay from C_{in} to C_{out} of final AND/OR gate in k -bit CLA block

An N -bit carry-lookahead adder is generally much faster than a ripple-carry adder for $N > 16$

Carry-Lookahead Adder (Crude) Complexity

For N -bit CLA with k -bit blocks:

$$A_{CLA} \approx (N/k - 1)(A_{AND_OR} + A_{pg} + A_{pg_block}) + NA_{FA}$$

- A_{pg} : Area of circuit generating all P_i, G_i
- A_{pg_block} : Area of circuit generating all $P_{i:j}, G_{i:j}$
- A_{AND_OR} : Area of AND/OR gates for carry computation in k -bit CLA block
- Approximate because some FA does not have to generate C_{out}

A carry-lookahead adder is higher complexity compared to ripple carry adder (scaling is still linear)

Main Idea of Parallel Prefix Adder

- Computes carry in (C_{i-1}) for each column, then computes sum:

$$S_i = (A_i \oplus B_i) \oplus C_{i-1}$$

- Computes G and P for 1-, 2-, 4-, 8-bit blocks, etc. until all G_i (carry in) known
- $\log_2 N$ stages

Parallel Prefix Adder: (Notation) Trick #1

- Carry in either *generated* in a column or *propagated* from a previous column
- Assume that column -1 holds C_{in} , so

$$G_{-1} = C_{\text{in}}, P_{-1} = 0$$

- Carry in to column i = carry out of column $i-1$:

$$C_{i-1} = G_{i-1:-1}$$

$G_{i-1:-1}$: generate signal spanning columns $i-1$ to -1

- Sum equation:

$$S_i = (A_i \oplus B_i) \oplus G_{i-1:-1}$$

- This trick allows to replace all Cs with corresponding Gs
- **Goal:** Quickly compute $G_{0:-1}, G_{1:-1}, G_{2:-1}, G_{3:-1}, G_{4:-1}, G_{5:-1}, \dots$ (called *prefixes*)

Parallel Prefix Adder: Trick #2


- Generate and propagate signals for a block spanning bits $i:j$:

$$G_{i:j} = G_{i:k} + P_{i:k} G_{k-1:j}$$


$$P_{i:j} = P_{i:k} P_{k-1:j}$$


- In words:
 - **Generate:** block $i:j$ will generate a carry if:
 - upper part ($i:k$) generates a carry or
 - upper part propagates a carry generated in lower part ($k-1:j$)
 - **Propagate:** block $i:j$ will propagate a carry if *both* the upper and lower parts propagate the carry

16-bit Parallel Prefix Adder

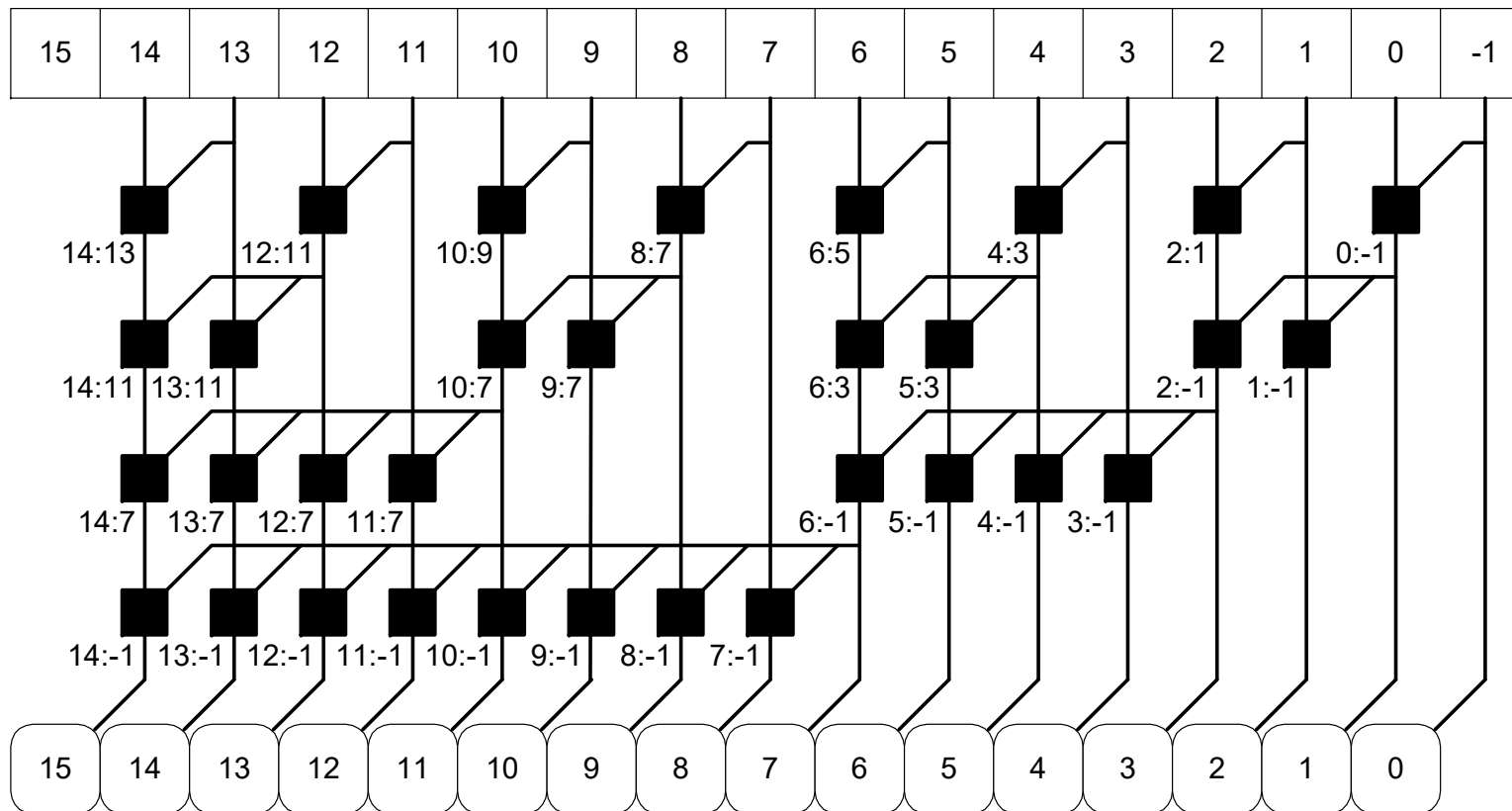

UCSB ECE 154A

 

 

Prefix Adder (Crude) Delay and Complexity

$$t_{PA} = t_{pg} + \log_2 N (t_{pg_prefix}) + t_{XOR}$$

- t_{pg} : delay to produce $P_i G_i$ (AND or OR gate)
- t_{pg_prefix} : delay of black prefix cell (AND-OR gate)

$$A_{PA} = NA_{pg} + N/2 \log_2 N (A_{pg_prefix}) + NA_{XOR}$$

- A_{pg} : area of circuit to produce $P_i G_i$ (AND or OR gate)
- A_{pg_prefix} : area of black prefix cell (AND-OR gate)
- A_{XOR} : area of 2 XOR gates

Adder (Crude) Delay Comparisons

Compare delay of: 32-bit ripple-carry, carry-lookahead, and prefix adders

- CLA has 4-bit blocks
- 2-input gate delay = 100 ps; full adder delay = 300 ps

$$t_{\text{ripple}} = Nt_{FA} = 32(300 \text{ ps})$$
$$= \mathbf{9.6 \text{ ns}}$$

$$t_{CLA} = t_{pg} + t_{pg_block} + (N/k - 1)t_{AND_OR} + kt_{FA}$$
$$= [100 + 600 + (7)200 + 4(300)] \text{ ps}$$
$$= \mathbf{3.3 \text{ ns}}$$

$$t_{PA} = t_{pg} + \log_2 N(t_{pg_prefix}) + t_{XOR}$$
$$= [100 + \log_2 32(200) + 100] \text{ ps}$$
$$= \mathbf{1.2 \text{ ns}}$$

Adder (Crude) Area Comparisons

Compare areas of: 32-bit ripple-carry, carry-lookahead, and prefix adders

- CLA has 4-bit blocks
- All logic gates have the same area A

$$\begin{aligned} A_{\text{ripple}} &= NA_{FA} = 32 \times 6A \\ &= \mathbf{192A} \end{aligned}$$

$$\begin{aligned} A_{CLA} &= (N/k - 1)(A_{\text{AND_OR}} + A_{pg} + A_{pg_block}) + NA_{FA} \\ &= (7)(2+2+7)A + 192A \\ &= \mathbf{269A} \end{aligned}$$

$$\begin{aligned} A_{PA} &= NA_{pg} + N/2 \log_2 N (A_{pg_prefix}) + NA_{XOR} \\ &= 32 \times 2A + 16 \log_2 32 \times 3A + 32 \times 2A \\ &= \mathbf{368A} \end{aligned}$$

Important Concepts to Remember

- Three types of adders: ripple-carry, carry-look ahead and prefix adder
- Different adders come with unique area-latency metrics
 - highlights typical area-latency tradeoffs in digital circuits
 - simple adders used in today's high-performance processors
 - FO4 delay: ~ 100 ps in 180 nm vs. ~ 1 ps in 5 nm

